



Faculty of Engineering & Technology

Department of Electrical & Computer Engineering

ENEE2103-CIRCUITS AND ELECTRONICS LABORATORY

Report#1

Experiment2: Circuit Laws and Theorems

Prepared by:

Hala Mohammed 1210312

Partners: Hamza Barhosh - 1210920

Ahmad Saqer - 1210085

Instructor: Dr. Mohammad Jehad Al Ju'Beh

Teaching Assistant: Eng. Eng. Rafah Rahhal

Section: 3

Date: 22-7-2024

Abstract

The main goal of our experiment is to connect various electrical circuits, understand them, and clearly grasp concepts such as Kirchhoff's laws, voltage and current divider rules, Thevenin and Norton theorems, and learn how to take voltage and current measurements for different circuits.

Table Of Contents

Abstract	4
Theory	1
Kirchhoff's Circuit Laws	1
1- Kirchhoff's Current low	1
2- Kirchhoff's Voltage low	1
Voltage and Current Division	2
1- Voltage Division	2
2- Current Division	3
Superposition	4
Thevenin and Norton equivalent circuits	5
1) Thevenin Equivalent Circuit	5
2) Norton Equivalent Circuit	6
Procedure and Discussion	7
A. KVL, KCL	7
- Theoretical	7
- practical	11
-Discussion	11
B. Voltage & Current Division	12
I. Voltage division	12
II. Current division	15
C. Superposition	18
D. Thevenin and Norton equivalent circuits	23
Conclusion	31
References	32
Appendix	33

Table Of Figures

Figure 1 :Node	1
Figure 2 :Voltage low	2
Figure 3 :Voltage Divider	3
Figure 4 :Current Divider	4
Figure 5 :Thevenin Equivalent Circuit	5
Figure 6 :Norton Equivalent Circuit	6

Tabel Of Tables

Table 1 :Voltages and Currents for Theoretical KVL, KCL circuits	10
Table 2 Table 2:Voltages and Currents for practical KVL, KCL circuits	11
Table 3 :Voltages for Theoretical voltage division circuits	13
Table 4 :Voltages for practical voltage division circuits	14
Table 5 :Currents for Theoretical Current division circuits	16
Table 6 :Currents for Practical Current division circuits	17
Table 7 :Voltages and Currents for Theoretical Superposition Circuit	21
Table 8 :Voltages and Currents for practical Superposition Circuit	22
Table 9 :Data for Theoretical Thevenin and Norton equivalent circuits	29
Table 10 :Data for practical Thevenin and Norton equivalent circuits	30

Theory

Kirchhoff's Circuit Laws

1- Kirchhoff's Current law

Kirchhoff's Current Law (KCL) is a key principle for analyzing electrical circuits. It basically says that at any point in a circuit where currents come together (node or junction), the total current flowing into that point must equal the total current flowing out.

KCL means:

The total current entering a node equals the total current leaving the node.

This concept helps figure out how currents are distributed in a circuit. By applying KCL to each junction in a circuit, and can set up equations that help to solve for unknown currents, and it can be tackled with methods like matrix calculations or nodal analysis. [1]


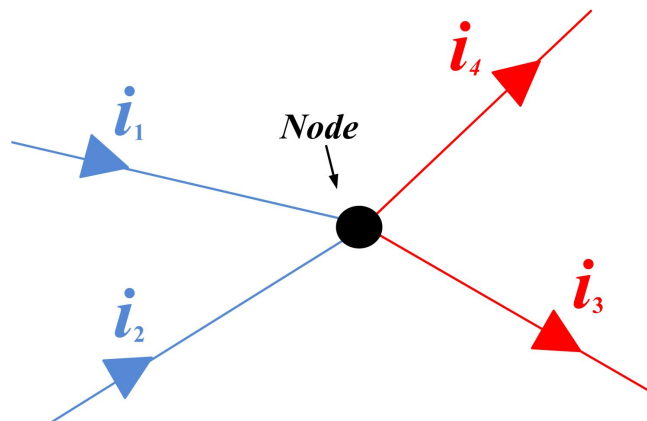


Figure 1:Node

2- Kirchhoff's Voltage law

Circuits with lumped parameters are analyzed using Kirchhoff's voltage and current laws. We are able to conduct a methodical study of any electrical network thanks to these laws and the voltage-current properties of the system's circuit parts. This section explains the voltage law of Kirchhoff.

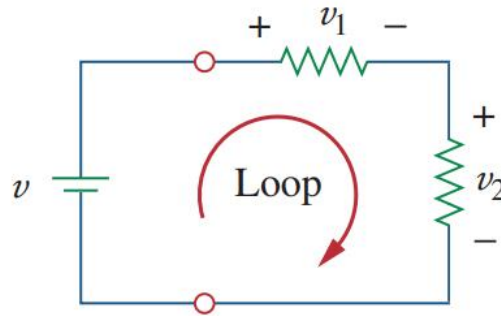The idea of a loop is central to KVL. A closed path in a circuit that doesn't pass through any nodes more than once is called a loop. Just begin at any node and follow a path across the circuit until you return to the starting point to construct a loop.[2]



$$KVL: -v + v_1 + v_2 = 0$$

Figure 2:Voltage law

Voltage and Current Division

1- Voltage Division

A voltage divider is a passive linear circuit that produces an output voltage (V_{out}) that is a fraction of its input voltage (V_{in}). This happens by distributing the input voltage among the components of the divider. A simple example is two resistors connected in series, with the input voltage applied across the pair and the output voltage taken from the junction between them.

Resistor voltage dividers are often used to create reference voltages or to reduce voltage levels for measurement purposes. They can also function as signal attenuators at low frequencies. For direct current (DC) and relatively low frequencies, a resistor-only voltage divider can be accurate enough. However, for applications requiring a wide frequency response, such as in oscilloscope probes, capacitive elements are added to the divider to compensate for load capacitance. In high-voltage measurement in electric power transmission, a capacitive voltage divider is used. [3]

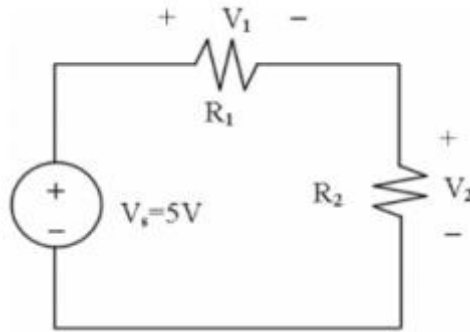


Figure 3: Voltage Divider

2- Current Division

A current divider is a straightforward linear circuit that produces an output current (I_X) that is a fraction of its input current (I_T). This process involves splitting the input current between the branches of the divider. The currents in these branches divide in such a way as to minimize the total energy expended.

There is one significant distinction between the formulas for current and voltage dividers. The branch's impedance is in the denominator of a current divider as opposed to the numerator of a voltage divider. This is because current travels through the least impedance channels in current dividers, resulting in an inverse relationship with impedance. In contrast, Kirchhoff's Voltage Law (KVL), which calls for dividing voltage decreases proportionate to the impedance, is the foundation of a voltage divider.

When two or more impedances are in parallel, the current splits between them inversely proportional to their impedances, as per Ohm's law. If the impedances are equal, the current will be split equally between the branches.[4]

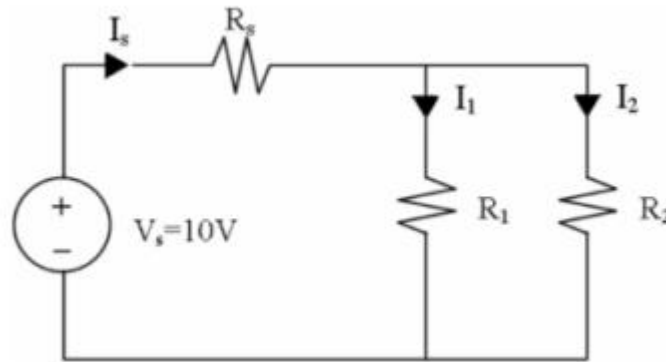


Figure 4: Current Divider

Superposition

The net response induced by two or more stimuli in any linear system is equal to the sum of the responses that would have been induced by each stimulus separately, according to the superposition principle, also called the superposition property. For input $(A + B)$ to produce response $(X + Y)$, if input A produces response X and input B produces response Y. [5]

To use the superposition principle, follow these steps:

1. All but one independent source should be turned off (deactivated).
2. Determine the output (current or voltage) from that source.
3. For each of the additional independent sources, repeat step 1.
4. Add up all of the voltages or currents from each independent source to find the total (voltage or current).

Thevenin and Norton equivalent circuits

1) Thevenin Equivalent Circuit

A single voltage source (Thevenin voltage) in series with a single resistor (Thevenin resistance) can be used to substitute a circuit with two terminals. The Thevenin resistance value is the corresponding resistance when viewed in retrospect.

network at the terminals for output. The open circuit voltage at the output terminals, with all voltage sources substituted with shorts and all current sources substituted with opens, is the value of the Thevenin voltage. [6]

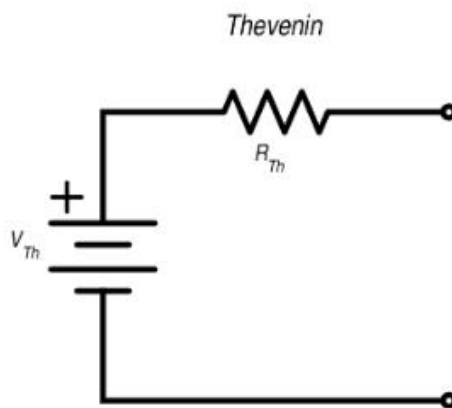


Figure 5: Thevenin Equivalent Circuit

2) Norton Equivalent Circuit

A single current source (Norton current) in parallel with a single resistor (Norton resistance) can be used to substitute a circuit with two terminals. The Norton resistance's value is the corresponding resistance when examining the

network at the terminals for output. The short circuit current at the output terminals, with every voltage source substituted by a short and every current source substituted by an open, is the Norton current. [7]

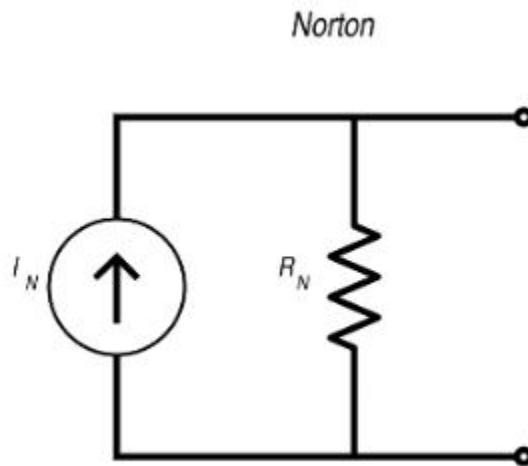



Figure 6:Norton Equivalent Circuit

Procedure and Discussion

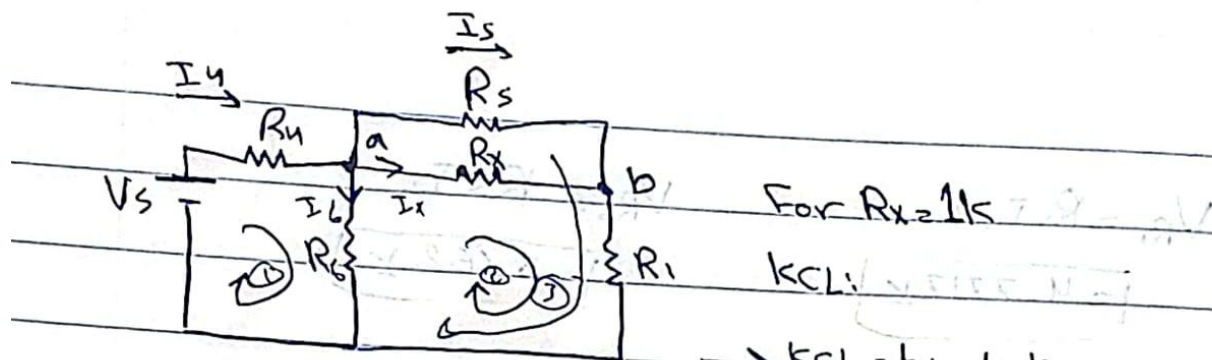A. KVL, KCL

- Hand Calculation

$R_5 = 3.3K$, $R_6 = 4.7K$, $R_1 = R_4 = R_X = 1K$, $V_s = 15V$



For $R_X = 1K$

KCL:

→ KCL at node b

$$I_1 = I_s + I_x \quad \text{--- (1)}$$

→ KCL at node a

$$I_6 = I_s + I_x + I_1$$

KVL:

→ KVL at loop 1:-

$$15 = 1K I_4 + 4.7K I_6 \quad \text{--- (2)}$$

→ KVL at loop 2

$$I_x 1K + I_1 1K - 4.7K I_6 = 0 \quad \text{--- (3)}$$

→ KVL at loop 3

$$3.3K I_s + 1K I_1 - 4.7K I_6 = 0 \quad \text{--- (4)}$$

Using ① & ④

$$I_x 1k + I_s 1k + I_x 1k - 4.7k I_6 = 0$$

$$I_x 2k + I_s 1k - 4.7 I_6 = 0 \quad \text{⑥}$$

Using ① & ⑤

$$3.3k I_s + 1k I_s + 1k I_x - 4.7k I_6 = 0$$

$$4.3k I_s + 1k I_x - 4.7k I_6 = 0 \quad \text{⑦}$$

Using ⑥ & ⑦

$$+ 2k I_x + I_s 1k - 4.7k I_6 = 0$$

$$- 2[4.3k I_s + 1k I_x - 4.7k I_6 = 0]$$

$$\Rightarrow 2k I_x + I_s 1k - 4.7k I_6 = 0$$

$$\text{④} - 8.6k I_s - 2k I_x + 9.4k I_6 = 0$$

$$\Rightarrow -7.6 I_s + 4.7 I_6 = 0$$

$$4.7 I_6 = 7.6 I_s$$

$$I_6 = 1.617 I_s \quad \text{⑧}$$

Using ⑤ & ⑥

$$2kI_x + I_s/k - 4.7(1.617I_s) = 0$$

$$2kI_x + I_s/k - 7.5999I_s = 0$$

$$2kI_x - 6.5999I_s = 0$$

$$2kI_x = 6.5999I_s$$

$$I_x = 3.29995I_s \quad \text{⑨}$$

Using ⑤ & ⑨ & ⑩

$$I_u = I_s + 3.29995I_s + 1.617I_s$$

$$I_u = 5.91695I_s \quad \text{⑩}$$

Using ⑩ & ⑧ & ③

$$I_s = 1kI_u + 4.7kI_s$$

$$I_s = 1k(5.91695I_s) + 4.7k(1.617I_s)$$

$$I_s = 5.91695kI_s + 7.5999kI_s$$

$$I_s = 13.51685kI_s$$

$$I_s = 1.10973 \text{ mA} \quad I_u = 6.566 \text{ mA} \quad I_x = 3.662 \text{ mA}$$

$$I_6 = 1.794 \text{ mA} \quad I_1 = 4.7717 \text{ mA}$$

$$V_{R1} = R_1 I_1$$

$$= 4.7717 \text{ V}$$

$$V_{R5} = R_5 I_5$$

$$= 3.662 \text{ V}$$

$$V_{R6} = R_6 I_6$$

$$= 8.4318 \text{ V}$$

$$V_{R4} = R_4 I_4$$

$$= 6.566 \text{ V}$$

$$V_{R_x} = R_x I_x$$

$$= 3.662 \text{ V}$$

$R_5 = 3.3\text{K}, R_6 = 4.7\text{K}, R_1 = R_4 = 1\text{K}, R_x = 0.5\text{K}, V_s = 15\text{V}$

Using the same calculation above but for $R_x = 0.5\text{K}$

Vs(Volt)	Rx	R1		R4		R5		R6		Rx	
		V1	I1	V4	I4	V5	I5	V6	I6	Vx	Ix
15V	1K	4.7717v	4.7717mA	6.566v	6.566mA	3.662v	1.10973mA	8.4318v	1.794mA	3.662v	3.662mA
15V	0.5K	5.4755v	5.4755mA	7.1466v	7.1466mA	2.378v	0.7205mA	7.85323v	1.6709mA	2.3775v	4.755mA

Table 1: Voltages and Currents for Theoretical KVL, KCL circuits

- practical

Initially, we verified that the resistance values provided corresponded to those in the lab handbook using a digital multimeter. After making sure of this, we assembled the circuit for this part, took measurements, and entered the results into a table. We accomplished this by measuring the voltage across the resistors in parallel and the current passing through them in series using the multimeter. We performed the tests again using a variable resistor set to 0.5 kilo-ohms in place of the 1 kilo-ohm resistor .

Vs(Volt)	Rx	R1		R4		R5		R6		Rx	
		V1	I1	V4	I4	V5	I5	V6	I6	Vx	Ix
15V	1K	4.7v	4.8mA	6.5v	8.8mA	4.7v	1.1mA	8.4v	1.3mA	3.8v	3.6mA
15V	0.5K	5.4v	5.5mA	7.1v	10.6mA	5.4v	0.8mA	7.8v	0.9mA	2.4v	4.7mA

Table 2Table 2: Voltages and Currents for practical KVL, KCL circuits

-Discussion



The two tables show how closely the values discovered attach the theoretical calculations. This shows the accuracy of the theory of Kirchhoff's laws, as we know. However, certain differences exist. For example, Table 2's I4 value varies because to circuit overloading.

B. Voltage & Current Division

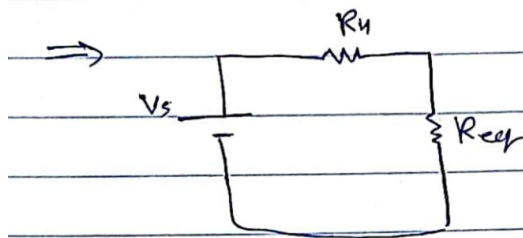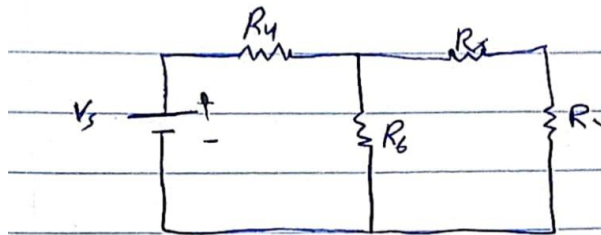I. Voltage division

- Hand Calculation

$R_5 = 3.3K$, $R_6 = 4.7K$, $R_1 = R_4 = 1K$, $R_x = 1K$, $V_s = 10V$



~~120312~~
120312

\Rightarrow For $R_x = 1k$.

$$R_{eq} = (R_1 + R_1) // R_6$$

$$= 1.4029 k\Omega$$

Voltage divider at R_4

$$V_{R_4} = \frac{R_4}{R_{eq} + R_4} \cdot V_s$$

$$= \frac{1}{1.4029 + 1} \cdot 10 = 4.1616V$$

Voltage divider at R_{eq}

$$V_{R_{eq}} = \frac{R_{eq}}{R_{eq} + R_u} \cdot V_s$$

$$= \frac{1.4029}{1.4029 + 1} \cdot 10$$

$$= 5.838V$$

use V_d
1210312

$$V_{R_6} = V_{R_{eq}} = 5.838V$$

Voltage divider for R_x

$$V_{R_x} = \frac{R_x}{R_x + R_1} \cdot V_{R_{eq}}$$

$$= \frac{1 \cdot 5.838}{1 + 1} = 2.919V$$

Voltage divider for R_1

$$V_{R_1} = \frac{R_1}{R_1 + R_x} \cdot V_{R_{eq}}$$

$$= \frac{1 \cdot 5.838}{1 + 1} = 2.919V$$

$R_5 = 3.3K$, $R_6 = 4.7K$, $R_1 = R_4 = 1K$, $R_x = 0.5K$, $V_s = 10V$

Using the same calculation above but for $R_x = 0.5K$

V_s (Volt)	R_x	V_1	V_4	V_6	V_x
10v	1K	2.919v	4.1616v	5.838v	2.919v
10v	0.5K	3.547v	4.679v	5.32v	1.773v

Table 3: Voltages for Theoretical voltage division circuits

- practical

Initially, we assembled the circuit for this part, took measurements, and entered the results into a table. We accomplished this by using the digital multimeter in parallel with a voltage meter, one may measure the voltage near the resistors in the circuit. We performed the tests again using a variable resistor set to 0.5 kilo-ohms in place of the 1 kilo-ohm resistor .

Vs(Volt)	Rx	V1	V4	V6	Vx
10v	1K	2.9v	4.1v	5.9v	2.9v
10v	0.5K	3.5v	4.6v	5.3v	1.8v

Table 4: Voltages for practical voltage division circuit

s


-Discussion

The two tables show how closely the values discovered attach the theoretical calculations. This shows the accuracy of the theory of Voltage division laws ,we know before are accurate.

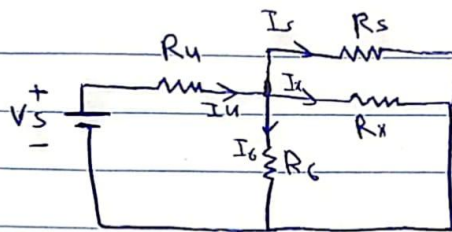II. Current division

- Hand Calculation

$R_5 = 3.3K$, $R_6 = 4.7K$, $R_1 = R_4 = 1K$, $R_x = 1k$, $V_s = 15V$



for $R_x = 1k\Omega$

$$R_{eq} = R_4 + (R_5 // R_x // R_6)$$

$$= 1.6597 k\Omega$$

~~15V~~

1210312

$$I_u = \frac{V_s}{R_{eq}} = \frac{15}{1.6597} \approx 6.025 mA$$

current through (R_5)

$$I_s = \frac{R_x // R_6}{(R_x // R_6) + R_5} \times I_u$$

$$= \frac{0.82456}{4.12456} \times 6.025$$

$$\approx 1.2045 mA$$

current divider (R_6)

$$I_6 = \frac{R_5 // R_x}{(R_5 // R_x) + R_6} \cdot I_u$$

$$= \frac{0.77}{5.47} \cdot 6.025$$

$$= 0.848 \text{ mA}$$

~~12.10312~~
12.10312

~~current divider (R_x)~~

current divider (R_x)

$$I_x = \frac{R_5 // R_6}{(R_5 // R_6) + R_x} \cdot I_u$$

$$= \frac{1.98375}{2.93875} \cdot 6.025$$

$$= 3.9748 \text{ mA}$$

$R_5 = 3.3\text{K}$, $R_6 = 4.7\text{K}$, $R_1 = R_4 = 1\text{K}$, $R_x = 0.5\text{k}$, $V_s = 15\text{V}$

Using the same calculation above but for $R_x = 0.5\text{K}$

$V_s(\text{volt})$	R_x	I_4	I_5	I_6	I_x
10	1K	6.025mA	1.2045mA	0.848mA	3.9748mA
10	0.5K	7.1556mA	0.8619mA	0.605mA	5.6885mA

Table 5: Currents for Theoretical Current division circuits

- practical

Initially, we assembled the circuit for this part, took measurements, and recorded the results in a table. We measured the current passing through the resistors in the circuit using a digital multimeter in series with a current meter. We then repeated the tests using a variable resistor set to 0.5 kilo-ohms in place of the 1 kilo-ohm resistor.

Vs(volt)	Rx	I4	I5	I6	Ix
10	1K	6mA	1.2mA	0.8mA	4.01mA
10	0.5K	7.2mA	0.86mA	0.6mA	5.7mA

Table 6: Currents for Practical Current division circuits


-Discussion

As we can see, the results in the two tables above are getting closer to one another. Our laboratory results are roughly equal to the result of our hand computations. By doing this, the circuit's current division validity is confirmed.

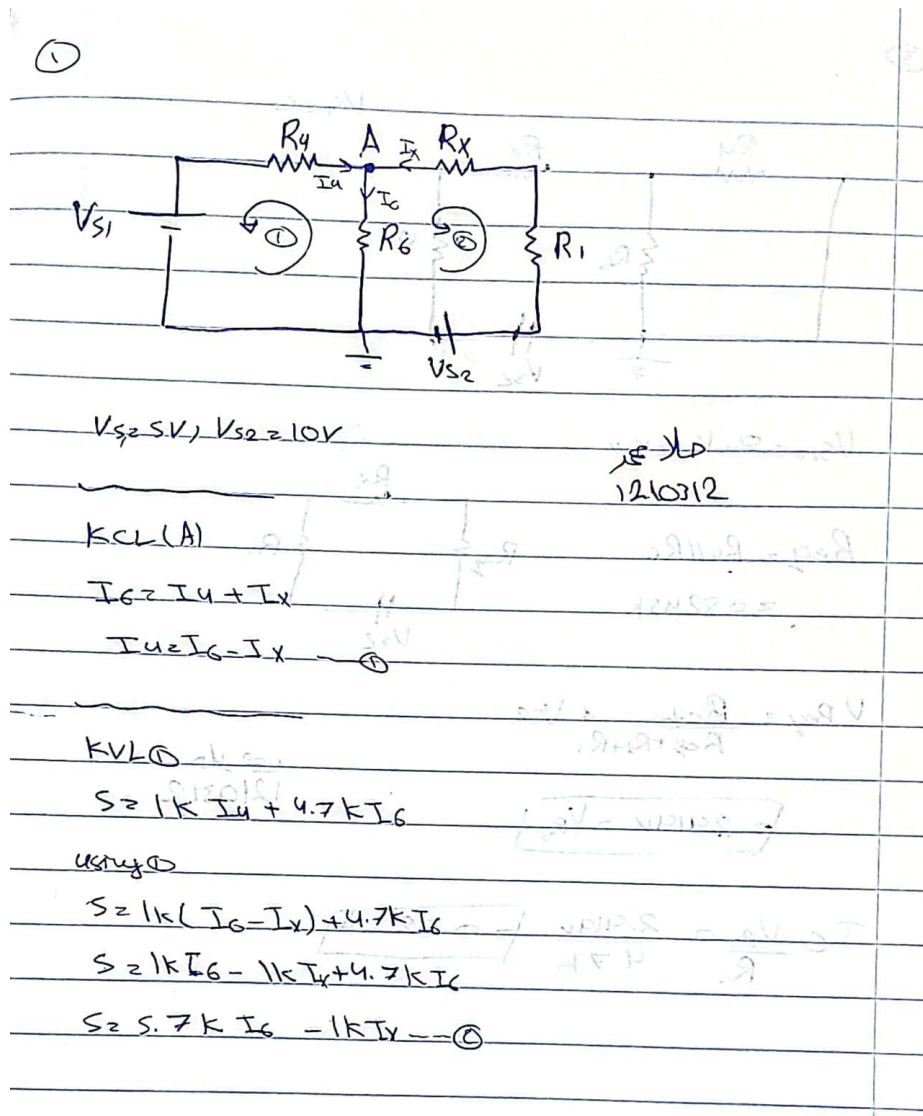C. Superposition

- Hand Calculation

$R_5 = 3.3K$, $R_6 = 4.7K$, $R_1 = R_4 = R_x = 1K$



②

KVL(2)

$$10 = I_x 1k + I_1 1k + 4.7k I_6$$

$$10 = 2k I_x + 4.7k I_6 \quad \text{--- ③}$$

~~3x2~~

$$2 [5 = 5.7k I_6 - 1k I_x]$$

$$+ 10 = 2k I_x + 4.7k I_6$$

$$10 = 11.4k I_6 - 2k I_x$$

$$10 = 2k I_x + 4.7k I_6$$


$$20 = 16.1k I_6$$

$$I_6 = 1.242 \text{ mA}$$

$$V_R = I_6 R_6$$


$$= 5.8385 \text{ V}$$

③

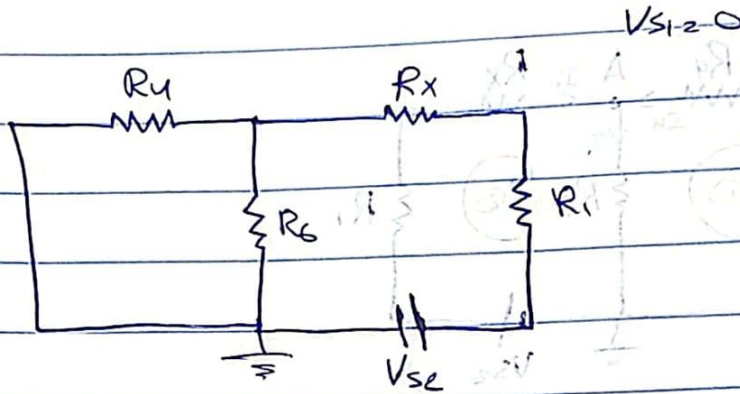

$$V_{S1} = 0 \text{ V}, V_{S2} = 10 \text{ V}$$
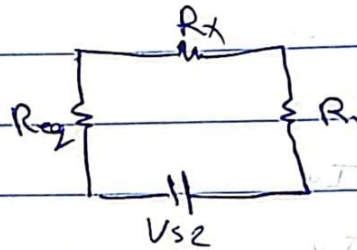
$$R_{eq} = R_4 \parallel R_6 \\ \approx 0.8245 \text{ k}$$




$$V_{Req} = \frac{R_{eq}}{R_{eq} + R_x + R_1} \cdot V_{S2}$$

$$\approx 2.919 \text{ V} \approx V_{R_6}$$


$$I_G = \frac{V_{R_6}}{R_6} = \frac{2.919 \text{ V}}{4.7 \text{ k}} \approx 0.62 \text{ mA}$$

(a)

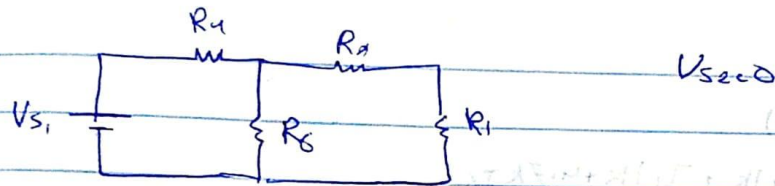

$$V_{S2} = 5V \text{ or } V_{S2} = 0$$
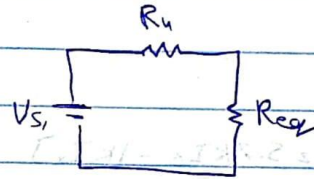
$$R_{eq} = (R_5 + R_1) \parallel R_6 \\ \approx 1.40299 \text{ k}$$



$$V_{Req} = \frac{R_{eq}}{R_{eq} + R_4} \cdot V_{S1}$$

$$\approx 2.919V \approx V_{R6}$$

$$I_6 = \frac{V_{R6}}{R_6} = \frac{2.919V}{4.7V} \approx 0.62 \text{ mA}$$

Vs1(volt)	Vs2(Volt)	V6(Volt)	I6(mA)
5	10	5.8385	1.242
0	10	2.919	0.62
5	0	2.919	0.62

Table 7: Voltages and Currents for Theoretical Superposition Circuit

- practical

In this part, firstly we connected the circuit needed with two voltage sources, Vs1 and Vs2, and then measured the voltage around R6 using a digital multimeter connected as a voltmeter in parallel to the resistor R6. Then we measured the current through the same resistor using another digital multimeter connected as an ammeter in series with the resistor. We then replaced Vs1 with a short circuit to kill Vs1, and we monitored the voltage and current as before. The final stage involved killing Vs2 by substituting a short circuit for Vs2, and then measuring the voltage and current as previously.

Vs1(volt)	Vs2(Volt)	V6(Volt)	I6(mA)
5	10	5.8	1.24
0	10	2.8	0.6
5	0	2.9	0.6

Table 8: Voltages and Currents for practical Superposition Circuit

-Discussion

As we can see from tables, the values obtained in the laboratory are closely matched with those from our hand calculations. This verifies the validity of superposition for the circuit. This close match proves that the theory behind superposition, as demonstrated in the theory section, is sound.

D. Thevenin and Norton equivalent circuits

- Hand Calculation

$R_5 = 3.3K$, $R_6 = 4.7K$, $R_1 = R_4 = R_x = 1K$, $V_{s1} = 5V$, $V_{s2} = 10V$

①

KCL (A)

$$I_6 = I_u + I_1$$

KVL ①

$$5 = 1K I_u + 4.7K I_6$$

$$5 = 1K I_u + 4.7K (I_u + I_1)$$

$$5 = 1K I_u + 4.7K I_u + 4.7K I_1$$

$$5 = 5.7K I_u + 4.7K I_1 \quad \text{--- ②}$$

KVL ②

$$10 = I_1 1K + I_1 1K + 4.7K I_6$$

$$10 = I_1 1K + I_1 1K + 4.7K (I_u + I_1)$$

$$10 = 2K I_1 + 4.7K I_u + 4.7K I_1$$

$$10 = 6.7K I_1 + 4.7K I_u \quad \text{--- ③}$$

(2)

② & ③

$$[525.7kI_u + 4.7kI_1] \cdot 4.7$$

$$[1026.7kI_1 + 4.7kI_u] \cdot 5.7$$

$$-23.52 = 26.79I_u - 22.09I_1$$

15 XD

$$57 = 38.14I_1 + 26.79I_u$$

1210312

$$33.5 = 16.1I_1$$


$$I_1 = 2.08 \text{ mA}$$

$$V_{R_1} = R_1 I_1$$

$$= 2.08 \text{ V}$$

③

$V_{ab1} =$

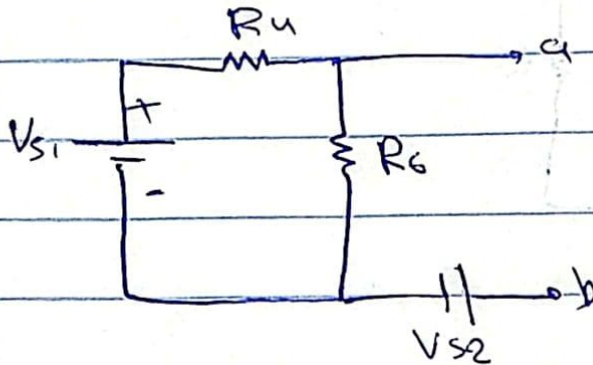

$$V_{R_6} = \frac{R_6}{R_6 + R_u} \cdot V_{s1}$$

$$= \frac{4.7 \text{ k}\Omega}{4.7 + 1}$$


$$= 4.1228 \text{ V}$$

$$V_{ab2} = V_{s2} - V_{R_2}$$

$$= 5.8772 \text{ V}$$

①

I_{sc} :-

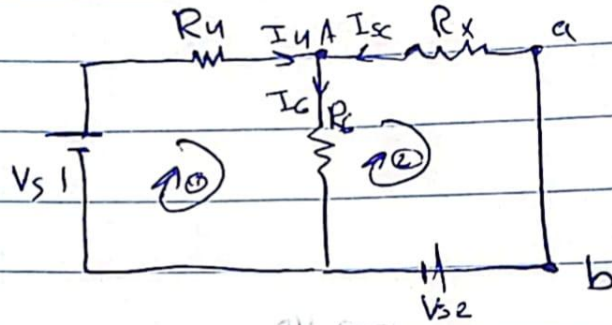

KCL(A)

$$I_G = I_{sc} + I_u \quad \text{--- ①}$$

KVL ①

$$5 = I_u \cdot 1k + 4.7k I_G$$

$$5 = I_u / k + 4.7k (I_{sc} + I_u)$$

$$5 = I_u / k + 4.7k I_{sc} + 4.7 I_u$$

$$5 = 5.7 I_u + 4.7k I_{sc} \quad \text{--- ②}$$

KVL ②

$$10 = 1k I_{sc} + 4.7k I_G$$

$$10 = 1k I_{sc} + 4.7k I_u \quad \text{--- ③}$$

③

② + ③

$$[5.2 \times 5.7 I_4 + 4.7 k I_{sc}] - 4.7$$

$$[10.2 \times 5.7 k I_{sc} + 4.7 k I_4] 5.7$$

$$-23.52 - 26.79 k I_4 - 22.09 I_{sc}$$


$$5.7 = 32.49 k I_{sc} + 26.79 k I_4$$

$$33.52 - 10.4 k I_{sc}$$

1210312

$$I_{sc} = 3.221 \text{ mA}$$

⑥

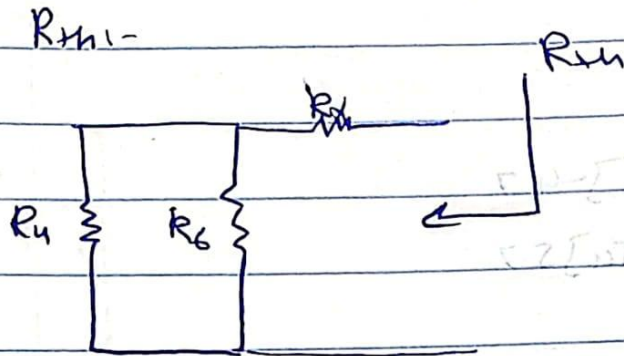

$$R_{th1} = (R_4 || R_6) + R_1$$


$$= 1.8246 \text{ k}\Omega$$

150 μ A
12V312



$$I_{th1} = \frac{V_{th}}{R_{th}} = \frac{5.8772 \text{ V}}{1.8246 \text{ k}\Omega}$$

$$= 3.221 \text{ mA}$$

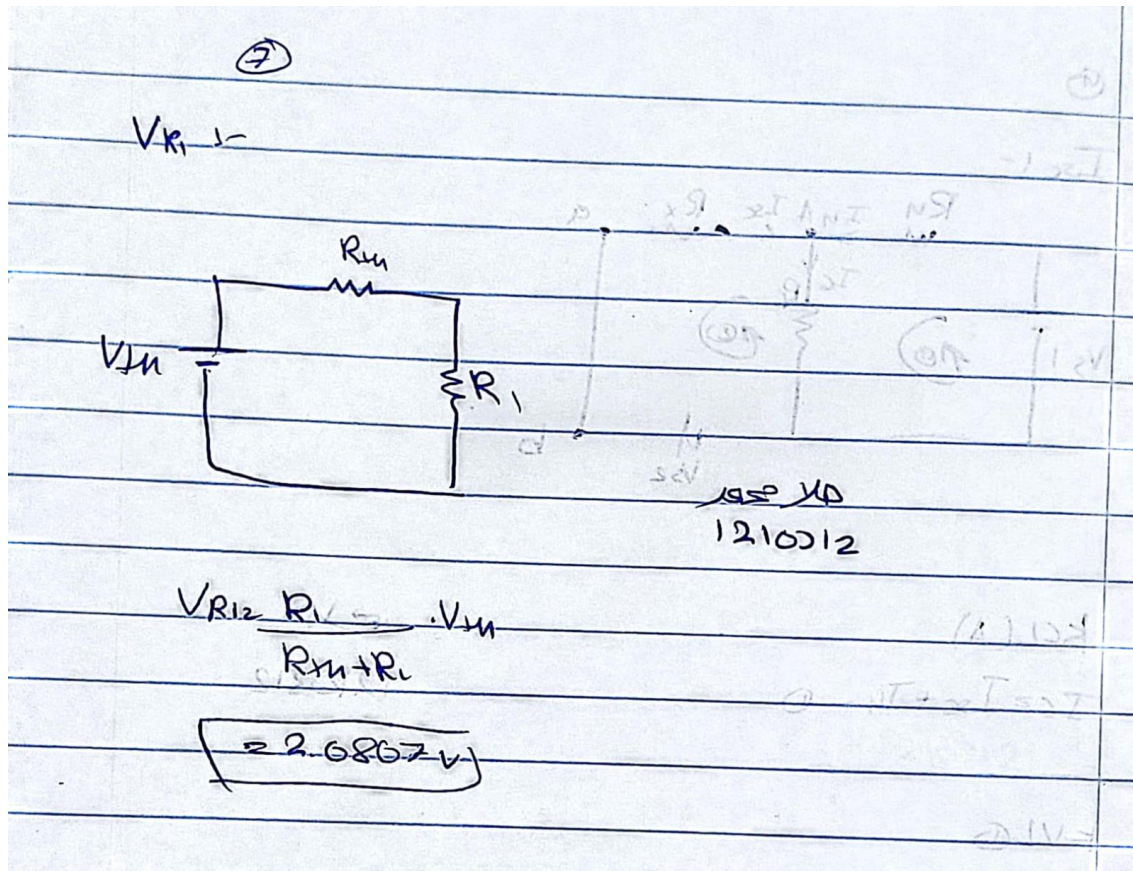

VR1	2.0807V
Voc	5.8772 V
Isc	3.221 mA
Rth	1.8246K

Table 9: Data for Theoretical Thevenin and Norton equivalent circuits

- practical

In this section, we first connected the circuit to two voltage sources, V_{s1} and V_{s2} , and then we measured the voltage surrounding $R1$ using a digital multimeter that was connected in parallel to $R1$ as a voltmeter. Once $R1$ was unplugged, we measured the voltage at the terminals (a, b) to which $R1$ was attached. The short-circuit current (I_{sc}) via the same terminals was then measured. Next, the voltage sources were cut off, and a short circuit was made to find R_{th} . Finally, we connected $R1$ and measured the voltage across it after connecting R_{th} and V_{th} and measuring the current via the short circuit.

Here we got negative values because we were reversing the polarities during the measurement process

VR1	-2V
Voc	-5.9V
Isc	-3.2 mA
Rth	1.8K

Table 10: Data for practical Thevenin and Norton equivalent circuits

-Discussion

Our experimental values closely match theoretical calculations, as tables demonstrate, demonstrating the accuracy of the Norton and Thevenin equivalent circuits. Thevenin equivalent produces the same output as the original circuit, and the manual calculations and lab findings match up nicely.

Conclusion

In conclusion, we demonstrated the validity of the Superposition theorem, the Thevenin and Norton equivalent circuits, the division rules for voltage and current, and Kirchhoff's laws (KVL and KCL). We gained knowledge on how to build practical circuits in the lab. We gained the know-how and abilities required to measure resistances, voltages, and currents while operating the equipment safely. The division rules for voltage and current, the applicability of the superposition theorem, and the operation of Kirchhoff's voltage and current laws were all verified. Finally, the circuits that corresponded to Thevenin and Norton were found.

References

- [1] <https://www.electronics-tutorials.ws/dccircuits/kirchhoffs-current-law.html>
accessed on 21/7/2027 at 8:08pm
- [2] <https://digilent.com/reference/learn/fundamentals/circuits/kirchhoffs-voltage-law/start>
accessed on 21/7/2027 at 8:14pm
- [3] https://en.wikipedia.org/wiki/Voltage_divider
accessed on 21/7/2027 at 7:51pm
- [4] https://en.wikipedia.org/wiki/Current_divider
accessed on 21/7/2027 at 7:56pm
- [5] https://en.wikipedia.org/wiki/Superposition_principle
accessed on 21/7/2027 at 8:24pm
- [6] https://en.wikipedia.org/wiki/Th%C3%A9venin%27s_theorem
accessed on 21/7/2027 at 8:29pm
- [7] https://en.wikipedia.org/wiki/Norton%27s_theorem
accessed on 21/7/2027 at 8:37pm

Appendix

Alhad sagor 1210085

16/7

11:00

Circuits & Electronics Lab

(Hamza Barhosh 1210920) ENEE2103

Hala Mohammed

ENEE2103

Experiment#2

Circuit Laws and Theorems

Objectives:

1. To use to measure the resistance, the voltage and the current.
2. To test the validity of the KVL and KCL laws.
3. To verify the validity of the voltage and current division rules.
4. To test the validity of the superposition theorem.
5. To determine the Thevinin and Norton equivalent circuits.

$$R_1 = .9832 \text{ k}\Omega$$

$$R_2 = .9936 \text{ k}\Omega$$

$$R_3 = 3.236 \text{ k}\Omega$$

$$R_4 = 4.7 \text{ k}\Omega$$

Equipment:

1. Digital Multimeter.
2. Feedback Prototype Board
3. DC power supply
4. Discrete Resistors, Resistance Decade Box

Pre-lab:

1. Simulate the circuits in the procedure section and determine the required values (set the parameters that must be assigned by the instructor in the procedure to proper values).
2. Verify if Simulation Results match the expected results

Procedure:

A. KVL, KCL

1. Measure the value of the resistances given to you by the lab instructor and make sure they match those in Fig. (2.1)
2. Connect the circuit of Fig (2.1). Consider $R_x = R_1 = R_4 = 1 \text{ k}\Omega$.
 $R_5 = 3.3 \text{ k}\Omega$, $R_6 = 4.7 \text{ k}\Omega$
3. Set the voltage source to 15 volts
4. Set the resistance decade box R_x to the value $1 \text{ k}\Omega$.
5. Measure and fill the values required in table 2.1 (value and sign according to the used sign convention).
6. Change the value of R_x to the half of the first value.
7. Repeat step 5
8. From your measurements verify the validity of KCL, KVL for the circuit.

Keep the circuit connected for the following part.

Table (2.1)

Vs	Pot	R1		R4		R5		R6		Rx	
		V1	I1	V4	I4	V5	I5	V6	I6	Vx	Ix
15V	Rx	4.7	4.8	6.5	8.8	1.1	8.4	1.3	3.8	3.6	
15V	0.5 Rx	5.4	5.5	7.1	10.6	3.4	18	7.8	1.9	2.4	4.7

overload \rightarrow 4.7

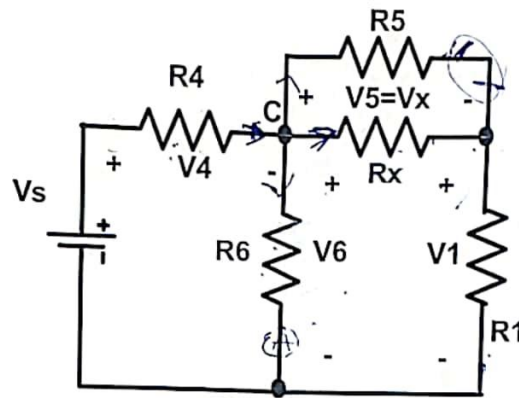


Fig (2.1)

B. Voltage & Current Division:**I. Voltage division**

1. In the circuit of Fig (2.1) disconnect the resistance R_5 from the circuit.
2. Measure the voltages on all the branches of the circuit.
3. Change R_x as shown in table 2.2 and repeat step 2 for all the given values.
4. In each case apply the resistors values into the voltage division formula
9. Do the measured values satisfy the voltage division rule? Keep the circuit connected for the following part.

Table (2.2)

Vs (volt)	Pot.	V1	V4	V6	Vx
10	R_x	2.9	4.1	5.9	2.9
10	$0.5R_x$	3.5	4.6	5.3	1.8

II. Current division

1. In the circuit of Fig (2.1) reconnect R_5 and replace R_1 by a short circuit and set R_x to its start value.
2. Measure the currents in all the resistive branches of the circuit and fill the values in table 2.3.
3. Change R_x as shown in table 3 and repeat step 2 for all the given values.
4. In each case apply the resistors values into the current division formula
5. Do the measured values satisfy the theoretical values of the current division rule?

Table (2.3)

Vs (volt)	Pot.	I_4	I_5	I_6	I_x
10	R_x	6.1	1.2	.8	4.01
10	$0.5R_x$	7.2	.86	.6	5.7

C. Superposition:

1. Connect the circuit of Fig (2.2).
2. Set the source V_{s1} to 5 volts and V_{s2} to 10 volts.
3. Set the variable resistor R_x to the value of 1K.
4. Measure the current and the voltage on R_6
5. Set V_{s1} to zero and V_{s2} to 10 volts measure the current and the voltage on R_6
6. Set V_{s1} to 5 volts and V_{s2} to zero and measure the current and the voltage on R_6
7. Define the relation between the three current values measured in (4,5,6)
8. Define the relation between the three voltage values measured in (4,5,6)

Table (2.4)

$V_{s1}(\text{volt})$	$V_{s2}(\text{volt})$	$V_6(\text{volt})$	$I_6(\text{mA})$
5	10	5.8	1.24
0	10	2.8	0.6
5	0	2.9	0.6

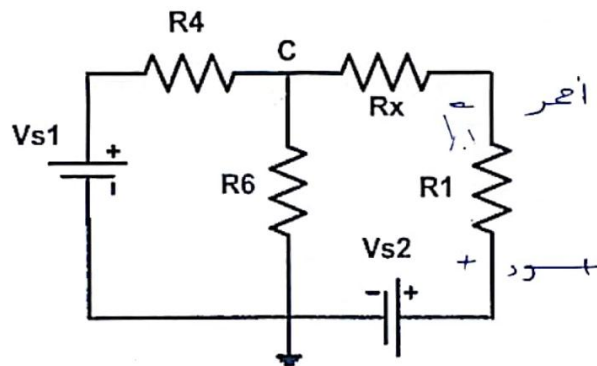


Fig (2.2)

D. Thevinin and Norton equivalent circuits:

1. Reconnect the circuit of Fig (2.2).
2. Set the V_{s1} to 5volts and V_{s2} to 10 volts and measure voltage across R_1 . $V_1 = 2V_c$
3. Disconnect R_1 and measure the voltage on the terminals (a,b) where R_1 was connected as in Fig (2.3). [Voc- open circuit voltage] $V_1 = 5.9V_c$
4. Short circuit the terminals (a, b) and measure the current in the short circuit (I_{sc}). $I_{sc} = -3.2$
5. Disconnect the voltage sources and short circuit the terminals where each source was connected. $R_1 = 8$

6. Measure the resistance from the terminals (a,b) ($R_{ab}=R_{th}$). *1.8*
7. Connect the voltage source in series with the variable resistance from the potentiometer (VR1) as in Fig (2.4), do not connect R1.
8. Set the voltage source to V_{oc} measured in step (3) and the variable resistance to R_{th} measured in step (4).
9. Measure the voltage on the opened terminals of the series connection. *5.9*
10. Short circuit the terminals of the series connection and measure the current in the short circuit. *3.2*
11. Define the relation between the voltage values measured in steps (3,9)
12. Define the relation between the current values measured in steps (4, 10)
13. Compute the ratio between the measured voltage V_{oc} and current I_{sc} in steps (3,4)
14. Define the relation between the computed value in step (13) and the resistance measured in step (5)
15. Connect the resistance R1 across terminal a-b of Fig. 2.4 and measure the voltage across it?
16. Compare voltage across R1 from step (15) to its value measured in step (2) *2.1*
17. What is the relation between the circuit of Fig.2.2 and the circuit of Fig.2.4 constructed in steps (7,8)? Refer to the electric variables on the port (a, b).
18. Compare the short circuit current value with the Norton current source determined by computation.

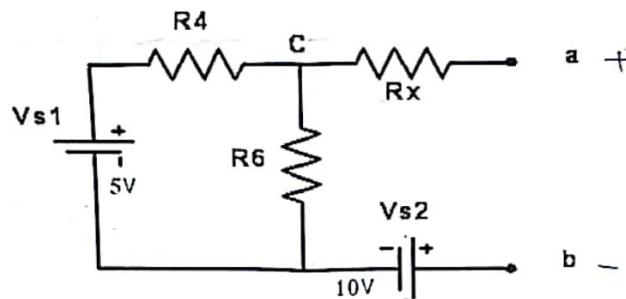


Fig (2.3)

$$R_{th} = \frac{V_{oc}}{I_{s.c}}$$

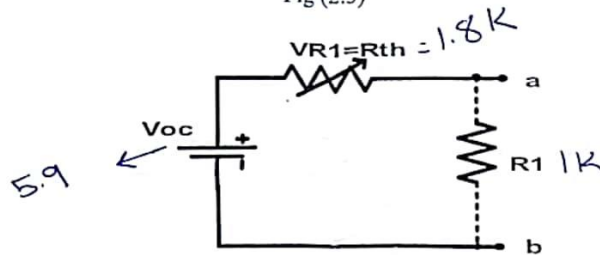


Fig (2.4)

Components List: $R1=R4=1\text{ k}\Omega$, $R5=3.3\text{ k}\Omega$, $R6=4.7\text{ k}\Omega$
Resistance Decade Box